

Université de Bretagne Occidentale
Département d'Informatique
Master 2 LSE



Adaptation et Ouverture
Introduction au langage VHDL

Ahcène Bounceur

2015

Plan du cours

1. Introduction au langage
2. Prise en main
3. Machine à états
4. Implémentation sur FPGA

Partie 1

INTRODUCTION AU LANGAGE

VHDL


- **V**HIC (V**er**y **H**igh-speed **I**ntegration **C**ircuit)
- **H**ardware
- **D**escription
- **L**anguage

1987 normalisé IEEE
1993 revu
1998 revu à nouveau
1998 IEEE std 1076

VHDL

- ❑ Conception/simulation de circuits ASIC/FPGA et test
- ❑ Développé aux USA dans les années 80, à l'initiative du département de la défense (initiative VHSIC)
- ❑ Syntaxe dérivée du langage ADA
- ❑ Extension : VHDL-AMS (VHDL-Analog and Mixed Systems).

Flot de conception

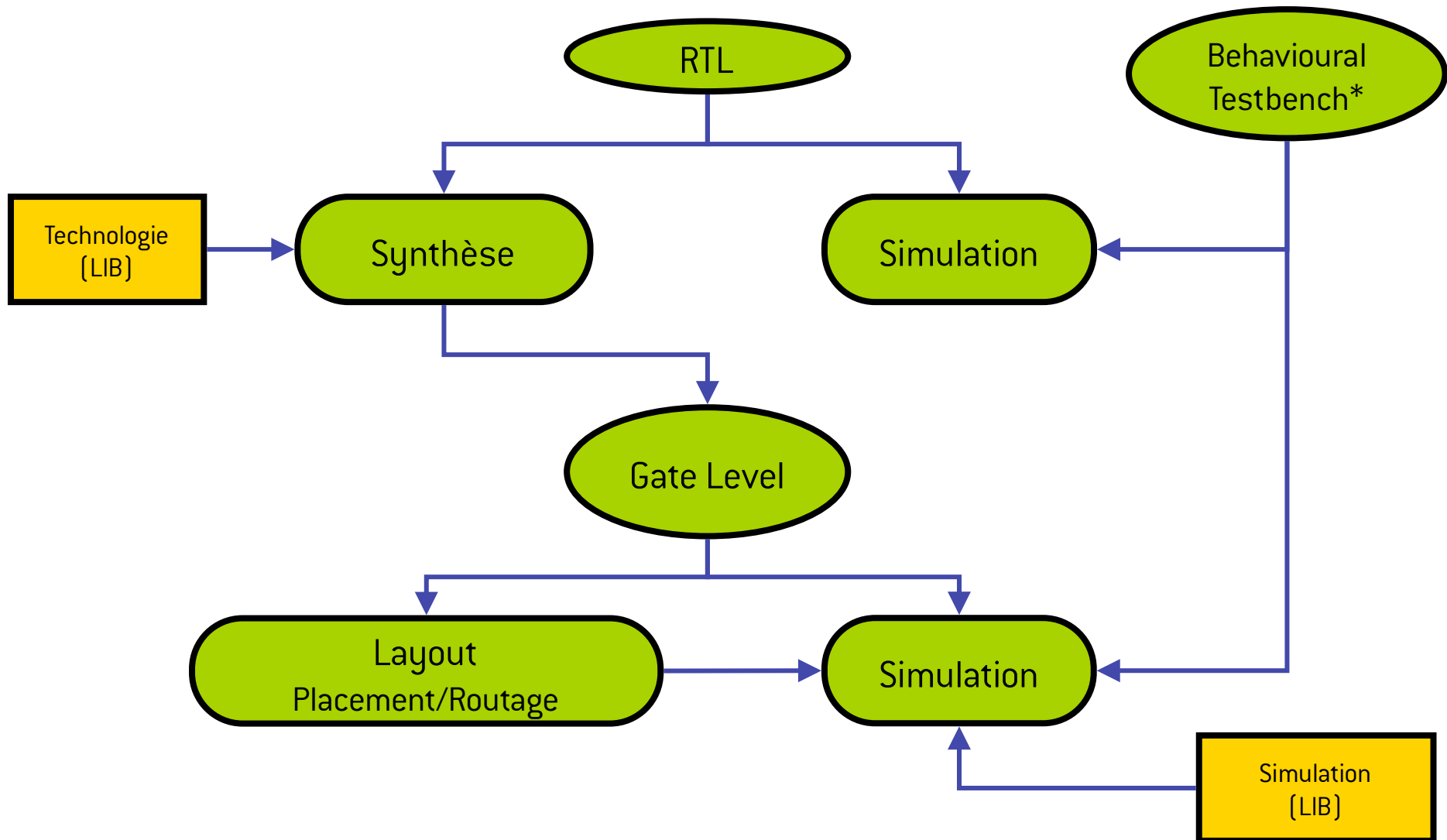

**Testbench en français Banc de test*

L'En-tête

```
Library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;
```

L'En-tête


```
entity DEMIADD is
port (
    A,B : in std_logic;
    R : in std_logic_vector(3 downto 0);
    SOMME, RETEN : out std_logic;
);
end DEMIADD;
```



L'Architecture

```
architecture ARCHI of DEMIADD is
-- déclarations préalables
begin
    SOMME <= A xor B;
    RETEN <= A and B;
end ARCHI;
```

Le Process

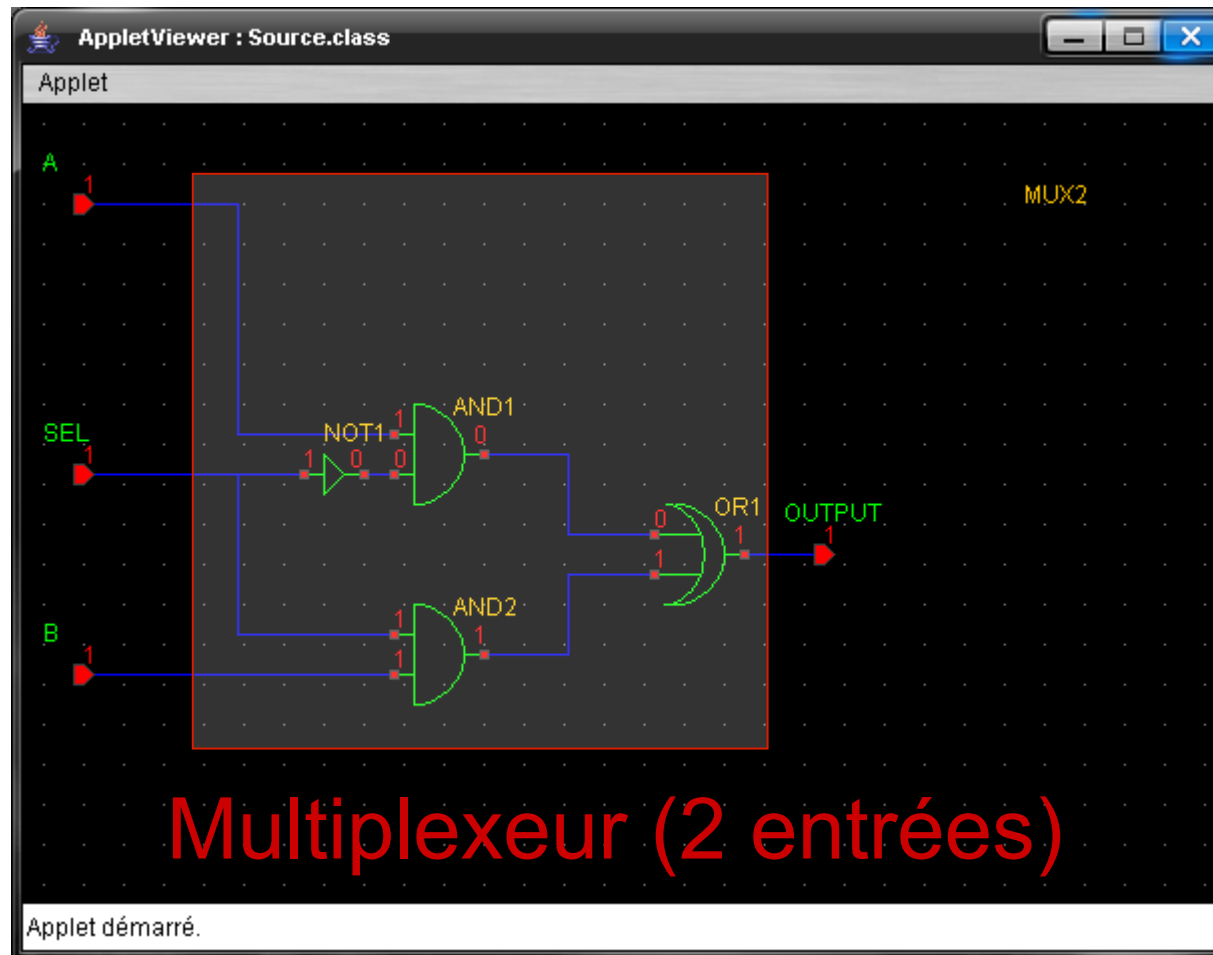

Le Process

```
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity MUX is
port (
    SEL,A,B : in std_logic;
    OUTPUT : out std_logic
);
end MUX;

architecture ARCHI of MUX is
begin
    MUXPROCESS : process (A,B,SEL)
    begin
        if SEL='1' then
            OUTPUT <= B;
        else
            OUTPUT <= A;
        end if;
    end process MUXPROCESS;
end ARCHI;
```

Le Process


```
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity MUX is
port (
    SEL,A,B : in std_logic;
    OUTPUT : out std_logic
);
end MUX;

architecture A of MUX is
begin
    MUXPROCESS : process (A,B,SEL)
    begin
        if SEL='1' then
            OUTPUT <= B;
        else
            OUTPUT <= A;
        end if;
    end process MUXPROCESS;
end A;
```

Le Process

MUXPROCESS : process (A, B, SEL)

 

Le Process


```
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity MUX is
port (
    SEL,A,B : in std_logic;
    OUTPUT : out std_logic
);
end MUX;

architecture A of MUX is
begin
    MUXPROCESS : process (A,B,SEL)
    begin
        if SEL='1' then
            OUTPUT <= B;
        else
            OUTPUT <= A;
        end if;
    end process MUXPROCESS;
end A;
```


Le Process

MUXPROCESS : process (B, SEL)

 

Librairie std_logic_arith
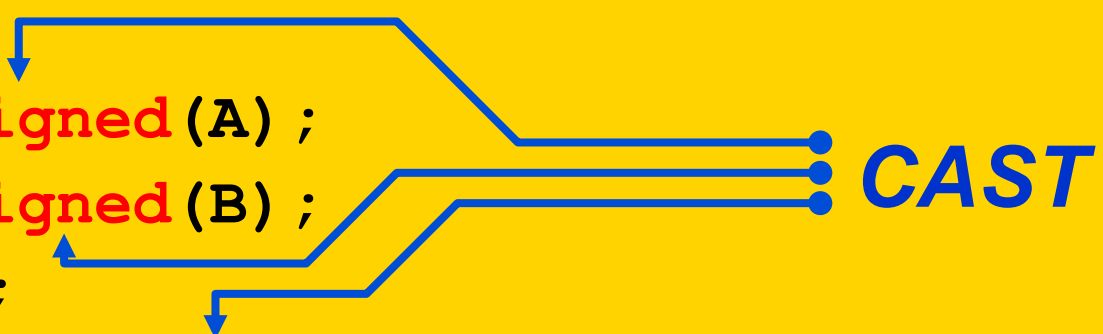
```
architecture archi of my_entity is
signal A,B,C : std_logic_vector(5 downto 0);
signal D,E,F : unsigned(5 downto 0)
begin
  D <= unsigned(A);
  E <= unsigned(B);
  F <= D+E;
  C <= std_logic_vector(F);
end;
```



CAST

| + | - | * | / | = |

| < | <= | > | >= | = | /= |

Agrégats et Concaténation

```
architecture archi of my_entity is
signal A,B,C : std_logic;
signal Z : std_logic_vector(1 downto 0)
signal S : std_logic_vector(7 downto 0)
Begin
    Z <= (A,B) ;
    S <= (7=>'1' , 5 downto 4=>Z , 6=>C , others=> '0') ;
    S <= '1' & C & Z & "0000" ;
    S(7) <= '1' ;
    S(6) <= C ;
    S(5 downto 4) <= Z ;
    S(3 downto 0) <= "0000" ;
end;
```

Attributs des signaux et Vecteurs

```
signal A : std_logic_vector(5 downto 0);
```

- `A'high` = 5
- `A'low` = 0
- `A'left` = 5
- `A'right` = 0
- `A'range` = 5 downto 0
- `A'reverse_range` = 0 to 5
- `A'length` = 6
- `A'ascending` = false

Attributs des signaux et Vecteurs

```
signal X : std_logic;
```

X'event = true quand X change de valeur

Règles d'écriture

- ❑ Un signal est défini par son type et sa taille
- ❑ Tout objet doit être déclaré avant d'être utilisé
- ❑ Les noms de signaux, les labels, ... doivent respecter les mêmes règles que les variables en langage soft (C/C++ et Java) et pas d'underscore (`_`) à la fin
- ❑ Le VHDL est insensible à la casse : `abc`, `Abc` ou `ABC` représentent le même nom
- ❑ Utiliser `--` pour introduire un commentaire et pas de commentaire sur plusieurs lignes
- ❑ Ne jamais utiliser `X <= X + Y`; si `X` et `Y` ne figurent pas dans la liste des signaux de la liste de sensibilité

L'écriture séquentielle et parallèle

```
if condition then
    -- séquence d'opérations
end if;
```

if

```
if condition then
    -- séquence 1 d'opérations
else
    -- séquence 2 d'opérations
end if;
```

L'écriture séquentielle et parallèle

if

```
if condition1 then
  -- séquence 1 d'opérations
elseif condition2 then
  -- séquence 2 d'opérations
elseif condition3 then
  -- séquence 3 d'opérations
else
  -- séquence n d'opérations
end if;
```

L'écriture séquentielle et parallèle

case

```
case expression is
when valeur1 =>
    -- séquence 1 d'opérations
when valeur2 to valeur5 =>
    -- séquence 2 d'opérations
when valeur6 | valeur8 =>
    -- séquence 3 d'opérations
when others =>
    -- séquence 4 d'opérations
end case;
```

L'écriture séquentielle et parallèle

for

```
signal X,Y : std_logic_vector(3 downto 0);  
--  
for I in 0 to 3 loop  
    Y(I) <= IP(3-I);  
end loop;
```


Assignment Concurrente

```
process (A, B, C, T)
begin
  if T>5 then
    Y <= A;
  elseif T<5 then
    Y <= B;
  else
    Y <= C;
  end if;
end process;
```

if



dans un process

hors process



```
Y <= A when T>5 else B when T<5 else C;
```

Assignment Concurrente

```
process (A, B, C, T)
begin
  case T is
    when 0 to 4 =>
      Y <= B;
    when 5 =>
      Y <= C;
    when others =>
      Y <= A;
  end case;
end process;
```

case

dans un process



hors process



```
with T select
Y <= B when 0 to 4, C when 5, A when others;
```

Variables & Signaux

variables

```
...  
signal A,B,P :  
  integer;  
begin  
  process (A,B)  
    variable vM,vN : integer  
  begin  
    vM := A;  
    vN := B;  
    P <= vM + vN;  
  end process;  
end ARCHI;
```


signaux

```
...  
signal A,B,P : integer;  
signal sM,sN : integer;  
begin  
  process (A,B,sM,sN)  
  begin  
    sM <= A;  
    sN <= B;  
    P <= sM + sN;  
  end process;  
end ARCHI;
```

Process CLOCKÉ

```
Library IEEE;  
...  
entity ...  
architecture ...  
signal CLK,RESET :std_logic;  
signal count : unsigned(3 downto 0);  
begin  
process (CLK)  
begin  
    if CLK'event and CLK='1' then  
        if RESET='1' then  
            count <= "0000";  
        elsif count>=9 then  
            count <= "0000";  
        else  
            count <= count + 1;  
        end if;  
    end if;  
end process;  
end architecture;
```

 - Machine à état SYNCHRONE
- Process réagissant sur front d'horloge




if rising_edge (CLK) then

Process CLOCKÉ

Éviter les if (pour la synthèse)
 
```
Library IEEE;  
...  
entity ...  
architecture ...  
signal CLK,RESET :std_logic;  
signal count : unsigned(3 downto 0);  
begin  
process (CLK)  
begin  
    wait until CLK'event and CLK='1';  
    if RESET='1' then  
        count <= "0000";  
    elsif count>=9 then  
        count <= "0000";  
    else  
        count <= count + 1;  
    end if;  
end process;  
end architecture;
```



wait until rising_edge (CLK) ;

Reset Asynchrone

```
begin
process (CLK, RESET)
Begin
    if RESET='1' then
        count <= "0000";
    elsif (CLK'event and CLK='1') then
        ...
    end if;
end process;
```

```
begin
process (CLK, RESET)
Begin
    if RESET='1' then
        count <= "0000";
    end if;
    wait until CLK'event and CLK='1';
    ...
end process;
```

Quelques Remarques

- ❑ Ne pas considérer le cas `rising_edge` et `falling_edge` au même temps
- ❑ Faire attention de bien écrire un process synchrone

```
wait until CLK'event and (CLK='1' or CLK='0');  
if CLK'event and (CLK='1' or CLK='0') then
```

```
wait until CLK'event  
if CLK'event then
```

```
wait until CLK='1';  
if CLK='1' then
```

Partie 2

PRISE EN MAIN

Les Fonctions combinatoires

Description par une table de vérité

ABCD	F
0000	0
0001	0
0010	0
0011	1
0100	0
0101	0
0110	0
0111	0
1000	1
1001	1
1010	1
1011	1
1100	1
1101	1
1110	1
1111	0

Description par une équation logique

$$F = \overline{A}B\overline{C} + \overline{A}C\overline{D} + \overline{A}B\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$$


Description et simplification par une table de Karnaugh

AB/CD	00	01	11	10
00			1	
01				
11	1	1		1
10	1	1	1	1



$$F = \overline{A}C\overline{D} + \overline{B}C\overline{D}$$

Les Fonctions combinatoires

Description logique en portes

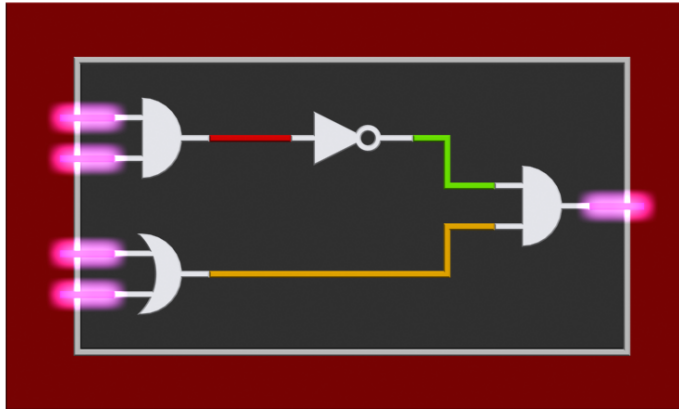


Description niveau transistor

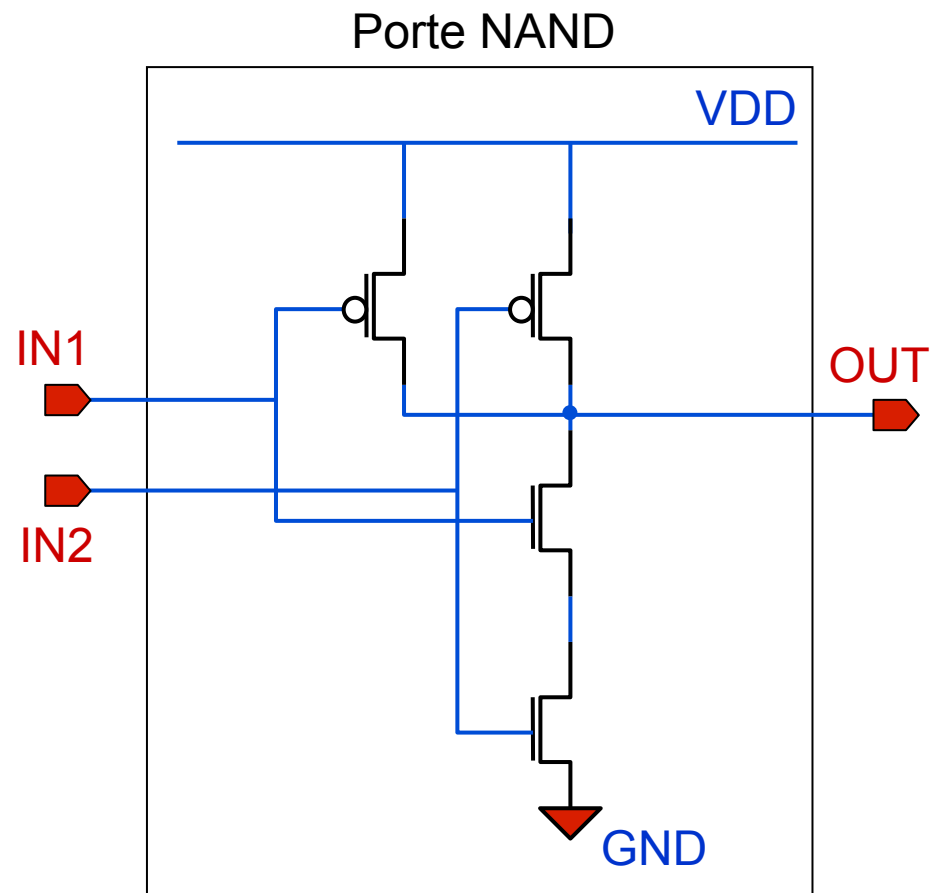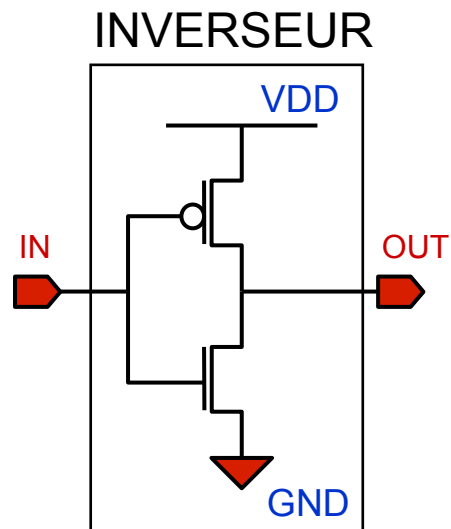


Description d'un circuit

- Code VHDL-AMS/Verilog-A
- Synthèse
- DFT
- Placement/Routage
- Implémentation FPGA/ASIC



Circuit à décrire

 

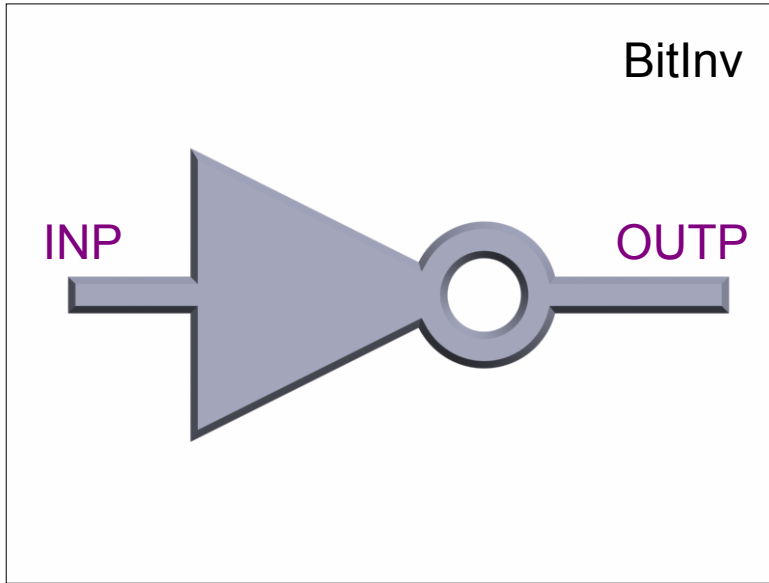

Entités

ENTREES
SORTIES

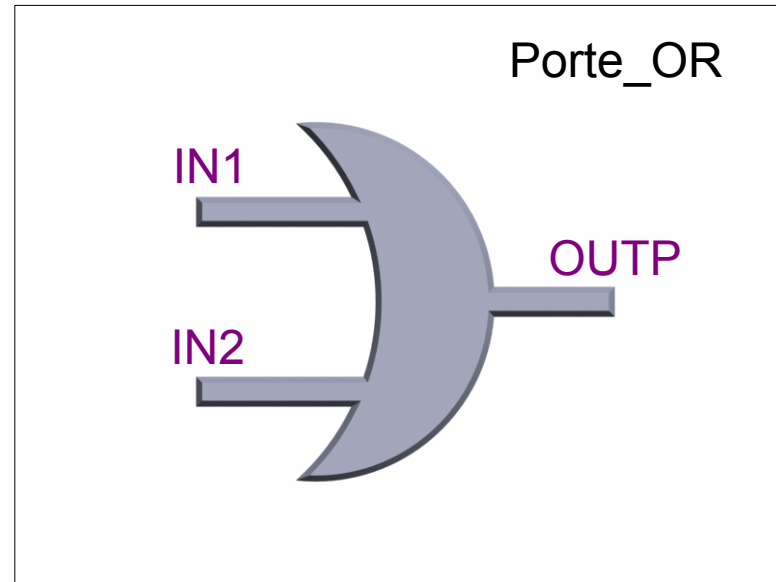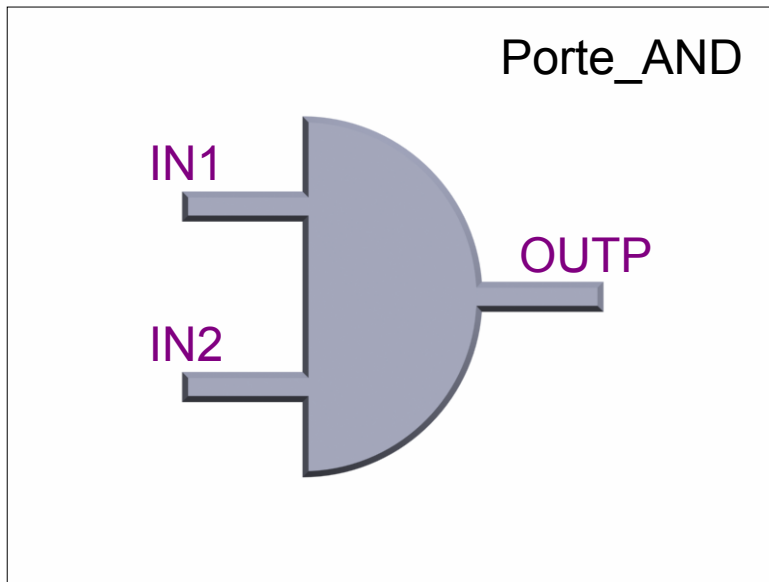

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;
```

Entité

```
entity Exple is
    port (
        CLK           : in  STD_LOGIC;
        RESET         : in  STD_LOGIC;
        INPUT          : in  STD_LOGIC_VECTOR(3 downto 0);
        OUTPUT         : out STD_LOGIC_VECTOR(3 downto 0);
    );
end Exple;
```

```
architecture A of Exple is
begin
    P_Exple : process
    begin
        if RESET='1' then
            OUTPUT <= "0000";
        end if;
        wait until CLK='1' and CLK'EVENT;
        OUTPUT <= INPUT;
    end process P_Exple;
end A;
```


Entité


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity Porte is
    port (
        INPUT    : in STD_LOGIC_VECTOR(3 downto 0);
        OUTPUT   : out STD_LOGIC_VECTOR(3 downto 0);
    );
end Porte;


architecture A of Porte is
begin
    P_Porte : process
    begin
        OUTPUT <= INPUT;
    end process P_Porte;
end A;

 architecture B of Porte is
begin
    P_Porte : process
    begin
        OUTPUT <= INPUT or '0';
    end process P_Porte;
end B;
```



 

Signaux (internes)

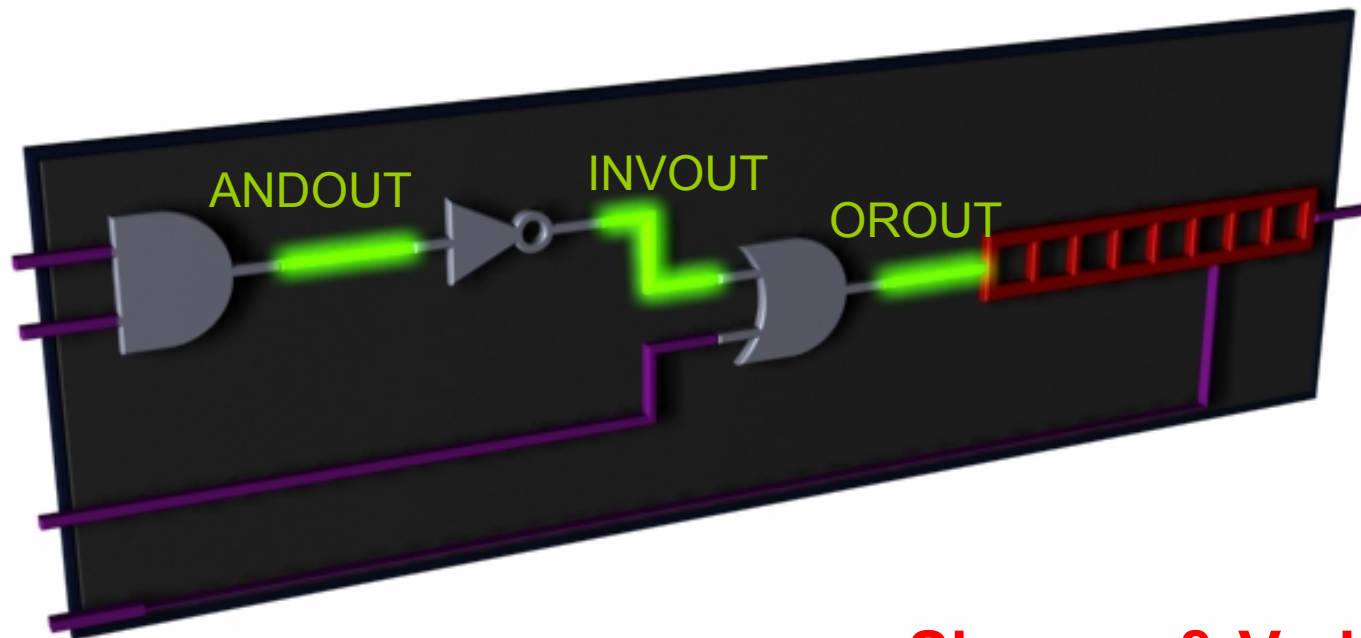



Signaux & Variables

```
Sig <= "0000"
```


```
Var := "0000"
```


Entrées/Sorties

 

 

MONCIRCUIT

 

 

Simulation : Bench

Porte AND

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity Porte_AND is
port (IN1      : in STD_LOGIC ;
      IN2      : in STD_LOGIC ;
      OUTP     : out STD_LOGIC);
end Porte_AND;

architecture A of Porte_AND is
begin
    OUTP <= IN1 and IN2;
end A;
```

Porte OR

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity Porte_OR is
port (IN1      : in STD_LOGIC ;
      IN2      : in STD_LOGIC ;
      OUTP     : out STD_LOGIC);
end Porte_OR;

architecture A of Porte_OR is
begin
    OUTP <= IN1 or IN2;
end A;
```


Inverseur

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

entity BitInv is
    port (    INP      : in STD_LOGIC ;
           OUTP       : out STD_LOGIC
           );
end BitInv;

architecture A of BitInv is
begin
    OUTP <= not INP;
end A;
```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;

entity Registre is
    port (
        RegIn          : in STD_LOGIC ;
        RegShift       : in STD_LOGIC ;
        RESET          : in STD_LOGIC ;
        CLK            : in STD_LOGIC ;
        RegOut         : out STD_LOGIC
    );
end Registre;

architecture ARCHI of Registre is
    type RegVecteur is array (0 to 7) of STD_LOGIC ;
    signal x : RegVecteur ;

begin
    Process_Registre : process(CLK)
    begin
        if (CLK'event and CLK='1') then
            if (RESET = '1') then
                for i in x'range loop
                    x(i) <= 'X';
                end loop ;
            elsif (RegShift = '1') then
                x(0) <= RegIn;
                for i in x'low to (x'high - 1) loop
                    x(i+1) <= x(i);
                end loop;
            end if;
        end if;
    end process Process_Registre;
    RegOut <= x(7);
end ARCHI;

```

Registre

```

library IEEE ;
use IEEE.std_logic_1164.ALL ;

entity MONCIRCUIT is
    port(
        -- Entrées/Sorties du circuit
    ) ;
end MONCIRCUIT;

architecture A of MONCIRCUIT is
-- Déclaration de composants utilisés
component Porte_AND
    port (
        IN1          : in STD_LOGIC ;
        IN2          : in STD_LOGIC ;
        OUTP         : out STD_LOGIC
    );
end component;
...
-- Signaux Internes
signal ANDOUT      : STD_LOGIC ;
signal INVOUT      : STD_LOGIC ;
signal OROUT       : STD_LOGIC ;
-- Les composants instanciés et leurs connections
begin

U1:Porte_AND port map (
    INPUT1  => MCIn1,
    INPUT2  => MCIn2,
    OUTPUT  => ANDOUT
);
...

end A;

```

Circuit

Bench

```
library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;

entity bench is
end bench;

architecture A of bench is
component moncircuit
    port(
        MCIn1          : in STD_LOGIC;
        MCIn2          : in STD_LOGIC;
        MCIn3          : in STD_LOGIC;
        MRegIn         : in STD_LOGIC;
        CLK            : in STD_LOGIC ;
        RESET          : in STD_LOGIC ;
        MCOut          : out STD_LOGIC ) ;
end component;

signal          sigINPUT1 : STD_LOGIC;
signal          sigINPUT2 : STD_LOGIC;
signal          sigINPUT3 : STD_LOGIC;
signal          sigRegIn  : STD_LOGIC;
signal          sigCLK    : STD_LOGIC := '0';
signal          sigRESET  : STD_LOGIC;
signal          sigOUTPUT : STD_LOGIC;

Begin
U1:MONCIRCUIT port map(sigINPUT1,sigINPUT2,sigINPUT3,sigRegIn,sigCLK,sigRESET,sigOUTPUT) ;

sigCLK <= not(sigCLK) after 100 ns;
sigRESET <= '1', '0' after 150 ns;
sigINPUT1 <= '0','0' after 250 ns;
sigINPUT2 <= '0','0' after 250 ns;
sigINPUT3 <= '0','0' after 250 ns;
sigRegIn <= '0','1' after 250 ns, '0' after 450 ns;
end;
```

Configuration du bench

```
library moncir_lib;


configuration bench_cfg_portes of bench is
  for A
    for U1 : moncircuit use entity moncir_lib.moncircuit(A) ;
    end for ;
  end for;
end bench_cfg_portes;
```

Partie 3

MACHINE À ÉTATS

Les Fonctions à mémoire

Description d'une fonction séquentielle

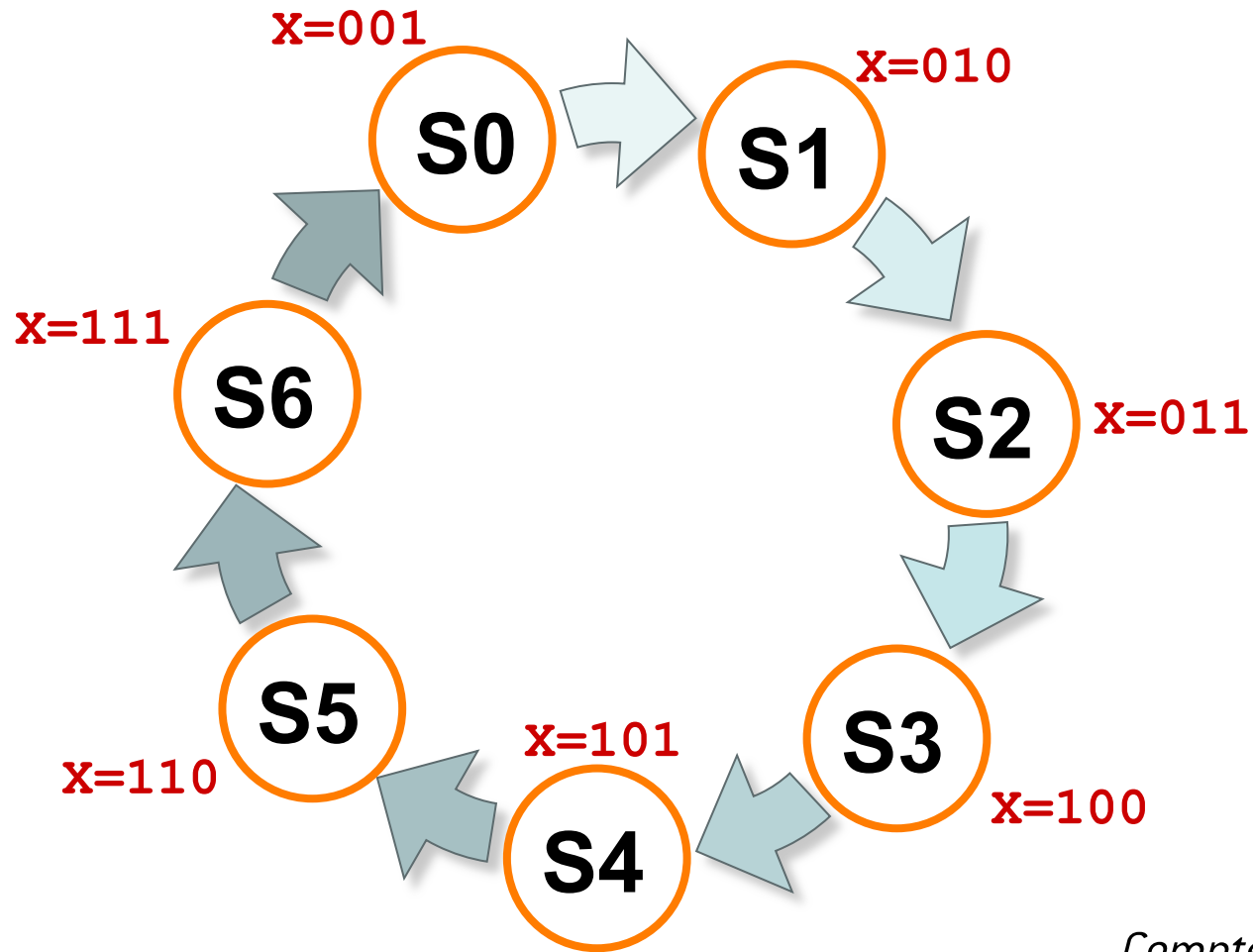

*Compteur synchrone
(passage d'un état au suivant sur un front d'horloge)*

FSM

```

library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;

entity FSM is
  port(
    CLK      : in STD_LOGIC;
    RESET    : in STD_LOGIC;
    ST       : out STD_LOGIC_VECTOR(2 downto 0)
  );
end FSM;

```

```

architecture A of FSM is
  type STATE is (S0,S1,S2,S3,S4,S5,S6);
  signal Current_State, Next_State : STATE ;

```

begin

```


  -- Processus de Mémorisation
  P_STATE:process (CLK)
  begin
    if (CLK='1' and CLK'EVENT ) then
      if (RESET='1') then
        Current_State <= S0 ;
      else
        Current_State <= Next_State ;
      end if ;
    end if;
  end process P_STATE;

```

```

  -- Processus Combinatoire
  P_FSM:process (Current_State)
  begin
    case Current_State is
      when S0 =>
        ST <= "001";
        Next_State <= S1;
      when S1=>
        ST <= "010";
        Next_State <= S2;
      when S2 =>
        ST <= "011";
        Next_State <= S3;
      when S3 =>
        ST <= "100";

```

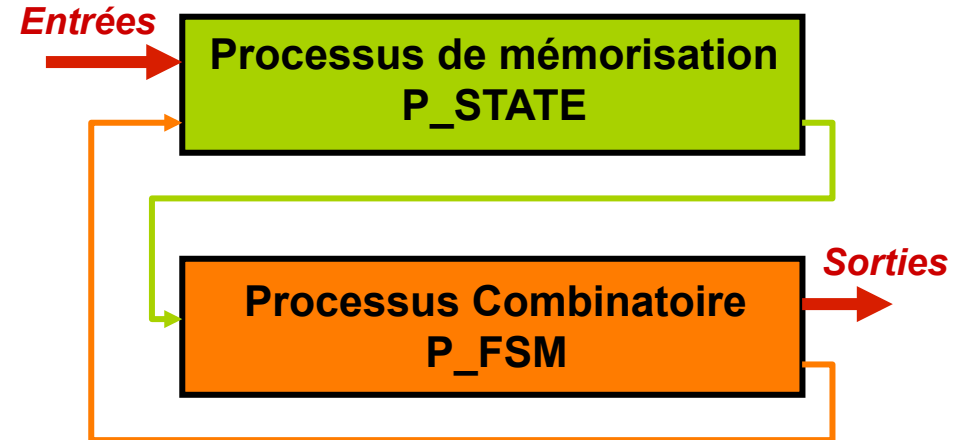

```

        Next_State <= S4;
      when S4 =>
        ST <= "101";
        Next_State <= S5;
      when S5 =>
        ST <= "110";
        Next_State <= S6;
      when S6 =>
        ST <= "111";
        Next_State <= S0;
    end case;
  end process P_FSM;

```

end A;


```
library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
entity BENCH_FSM is
end BENCH_FSM;
```

```
architecture A of BENCH_FSM is
```

```
component FSM
```

```
    port(
        CLK      : in STD_LOGIC;
        RESET    : in STD_LOGIC;
        ST       : out STD_LOGIC_VECTOR(2 downto 0)
    );
```

```
end component;
```

```
signal      sigCLK      : STD_LOGIC := '0';
signal      sigRESET    : STD_LOGIC;
signal      sigST       : STD_LOGIC_VECTOR(2 downto 0);
```

```
begin
```

```
U1:FSM port map(CLK,RESET,ST);
```


```
sigCLK <= not(CLK) after 100 ns;
```

```
sigReset <= '1',
            '0' after 150 ns ;
```

```
end;
```


Bench de la FSM (Simulation)

Simulation

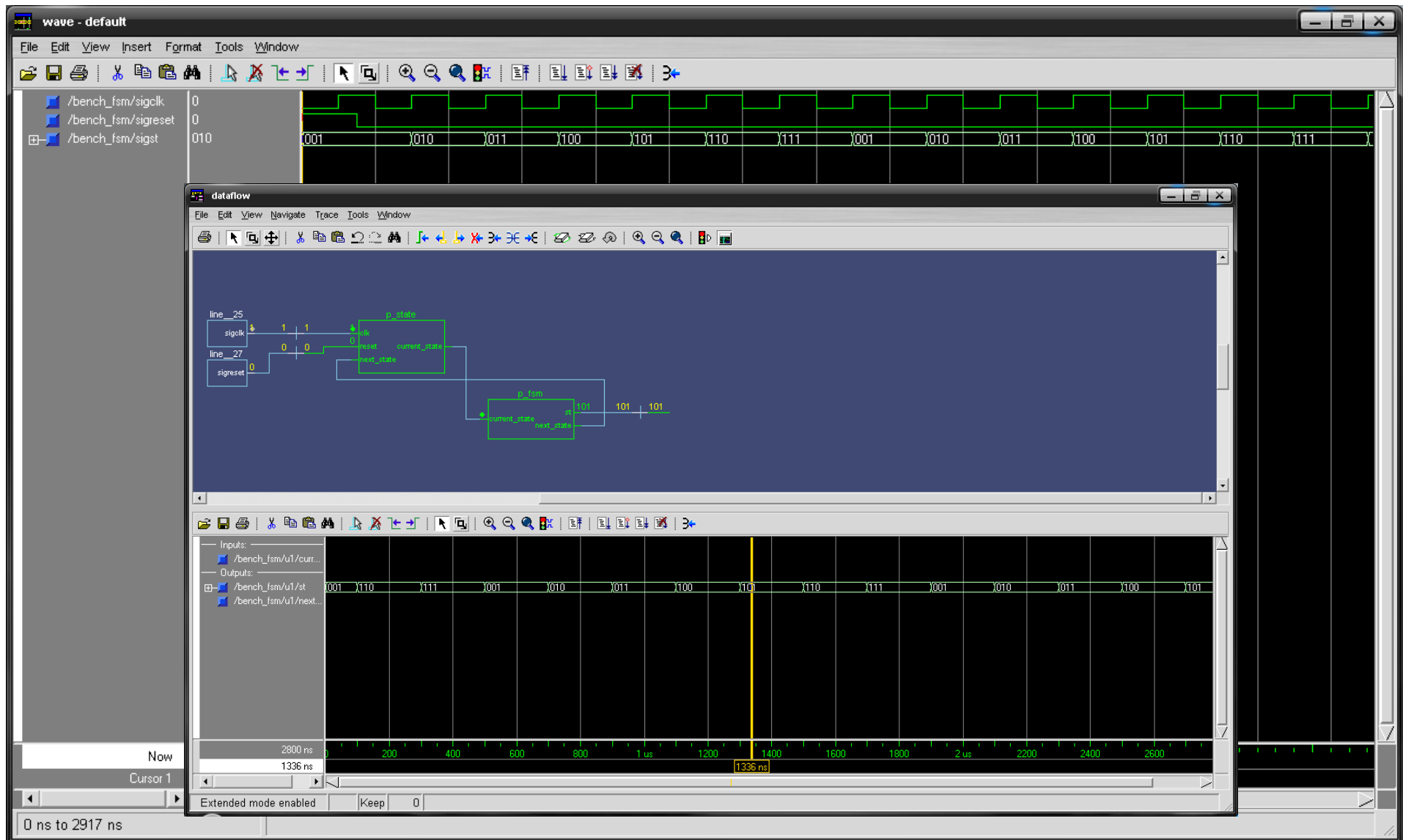

Les Fonctions à mémoire

Description d'une fonction séquentielle

 

*Compteur synchrone
(passage d'un état au suivant sur un front d'horloge)*

```

library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;

entity FSM is
    port(
        CLK          : in STD_LOGIC;
        RESET        : in STD_LOGIC;
        CTRL         : in STD_LOGIC;
        ST           : out STD_LOGIC_VECTOR(2 downto 0)
    );
end FSM;

```

```

architecture A of FSM is
    type STATE is (S0,S1,S2,S3,S4,S5,S6);
    signal Current_State, Next_State : STATE ;

```

```

begin
    -- Processus de Mémorisation
    P_STATE:process(CLK)
    begin
        if (CLK='1' and CLK'EVENT ) then
            if (RESET='1') then
                Current_State <= S0;
            else
                Current_State <= Next_State ;
            end if ;
        end if;
    end process P_STATE;

    -- Processus Combinatoire
    P_FSM:process(Current_State,CTRL)
    begin
        case Current_State is
            when S0 =>
                ST <= "000";
                if CTRL='1' then
                    Next_State <= S1;
                else
                    Next_State <= S0;
                end if;

```

FSM

```

        when S1=>
            ST <= "001";
            Next_State <= S2;
        when S2 =>
            ST <= "010";
            Next_State <= S3;
        when S3 =>
            ST <= "011";
            Next_State <= S4;
        when S4 =>
            ST <= "000";
            if CTRL='1' then
                Next_State <= S5;
            else
                Next_State <= S4;
            end if;
        when S5 =>
            ST <= "101";
            Next_State <= S6;
        when S6 =>
            ST <= "111";
            Next_State <= S0;
    end case;
    end process P_FSM;
end A;

```

```
library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
entity BENCH_FSM is
end BENCH_FSM;
```

```
architecture A of BENCH_FSM is
```

```
component FSM
```

```
    port(
        CLK      : in STD_LOGIC;
        RESET    : in STD_LOGIC;
        CTRL     : in STD_LOGIC;
        ST       : out STD_LOGIC_VECTOR(2 downto 0)
    );
```

```
end component;
```

```
signal    sigCLK      : STD_LOGIC := '0';
signal    sigRESET    : STD_LOGIC;
signal    sigCTRL     : STD_LOGIC := '0';
signal    sigST       : STD_LOGIC_VECTOR(2 downto 0);
```

```
begin
```

```
U1:FSM port map(sigCLK,sigRESET,sigCTRL,sigST);
```


```
sigCLK <= not(sigCLK) after 100 ns;
```

```
sigReset <= '1',
            '0' after 150 ns ;
```

```
end;
```

Bench 1

Simulation

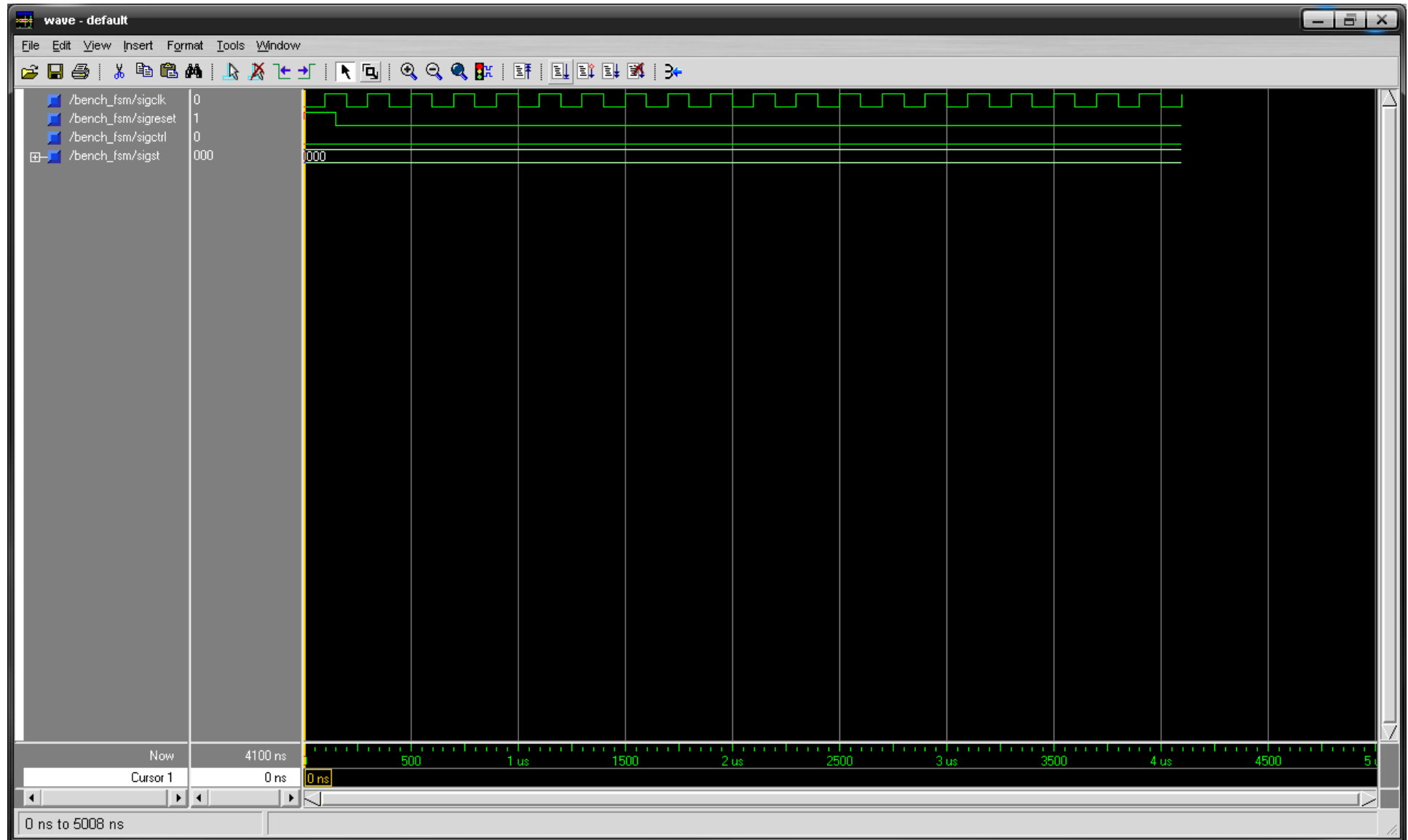

```

library IEEE ;
use IEEE.std_logic_1164.ALL ;
use IEEE.STD_LOGIC_ARITH.ALL;

entity BENCH_FSM is
end BENCH_FSM;

architecture A of BENCH_FSM is

component FSM
    port(
        CLK          : in STD_LOGIC;
        RESET        : in STD_LOGIC;
        CTRL         : in STD_LOGIC;
        ST           : out STD_LOGIC_VECTOR(2 downto 0)
    );
end component;

signal          sigCLK          : STD_LOGIC := '0';
signal          sigRESET        : STD_LOGIC;
signal          sigCTRL         : STD_LOGIC := '0';
signal          sigST           : STD_LOGIC_VECTOR(2 downto 0);

begin

U1:FSM port map(sigCLK,sigRESET,sigCTRL,sigST);

sigCLK <= not(sigCLK) after 100 ns;

sigReset <= '1',
           '0' after 150 ns ;


sigCTRL <= '0',
           '1' after 650 ns,
           '0' after 750 ns,
           '1' after 2450 ns,
           '0' after 2550 ns;

end;

```


Bench 2

Simulation

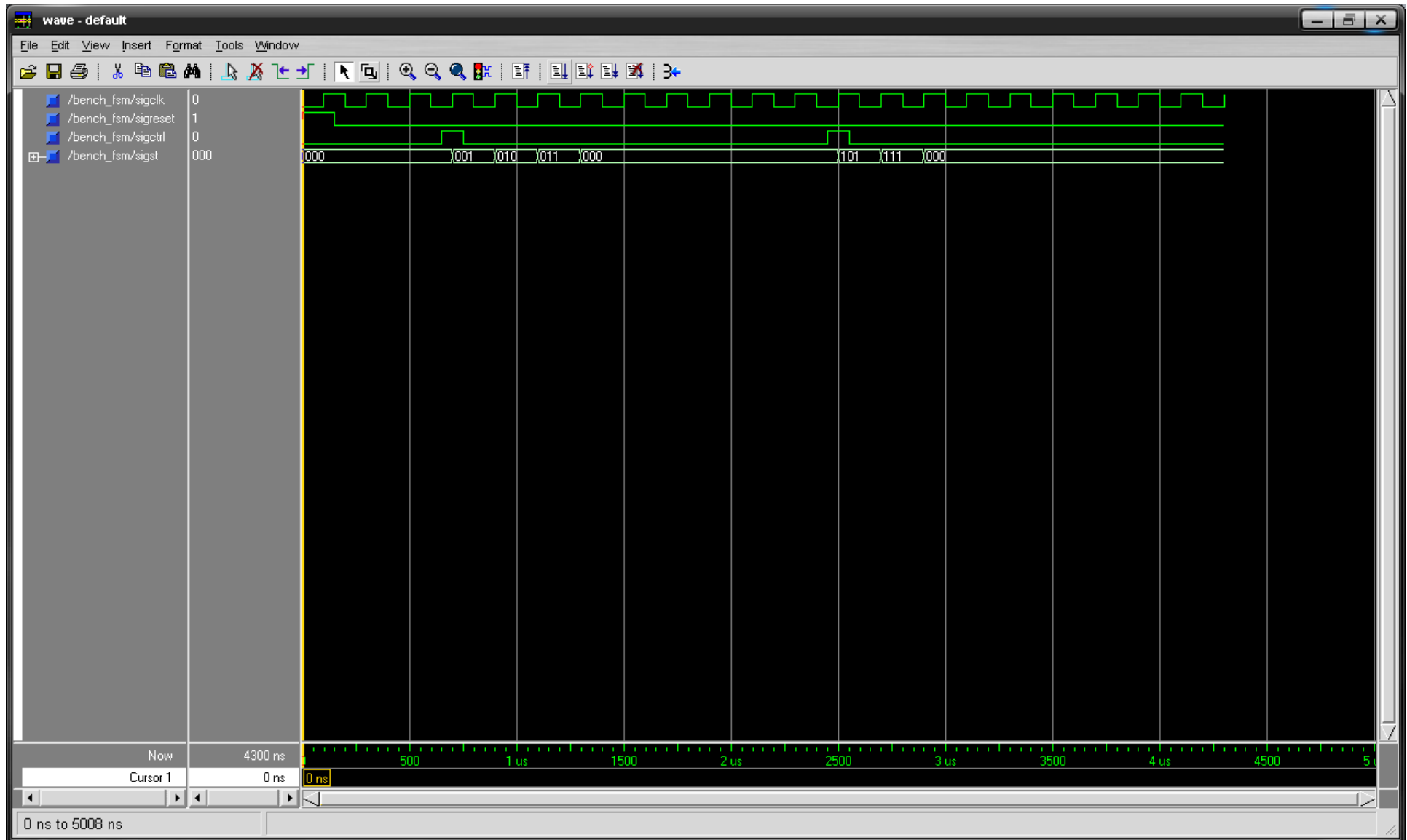

Exercice

Description d'une fonction séquentielle

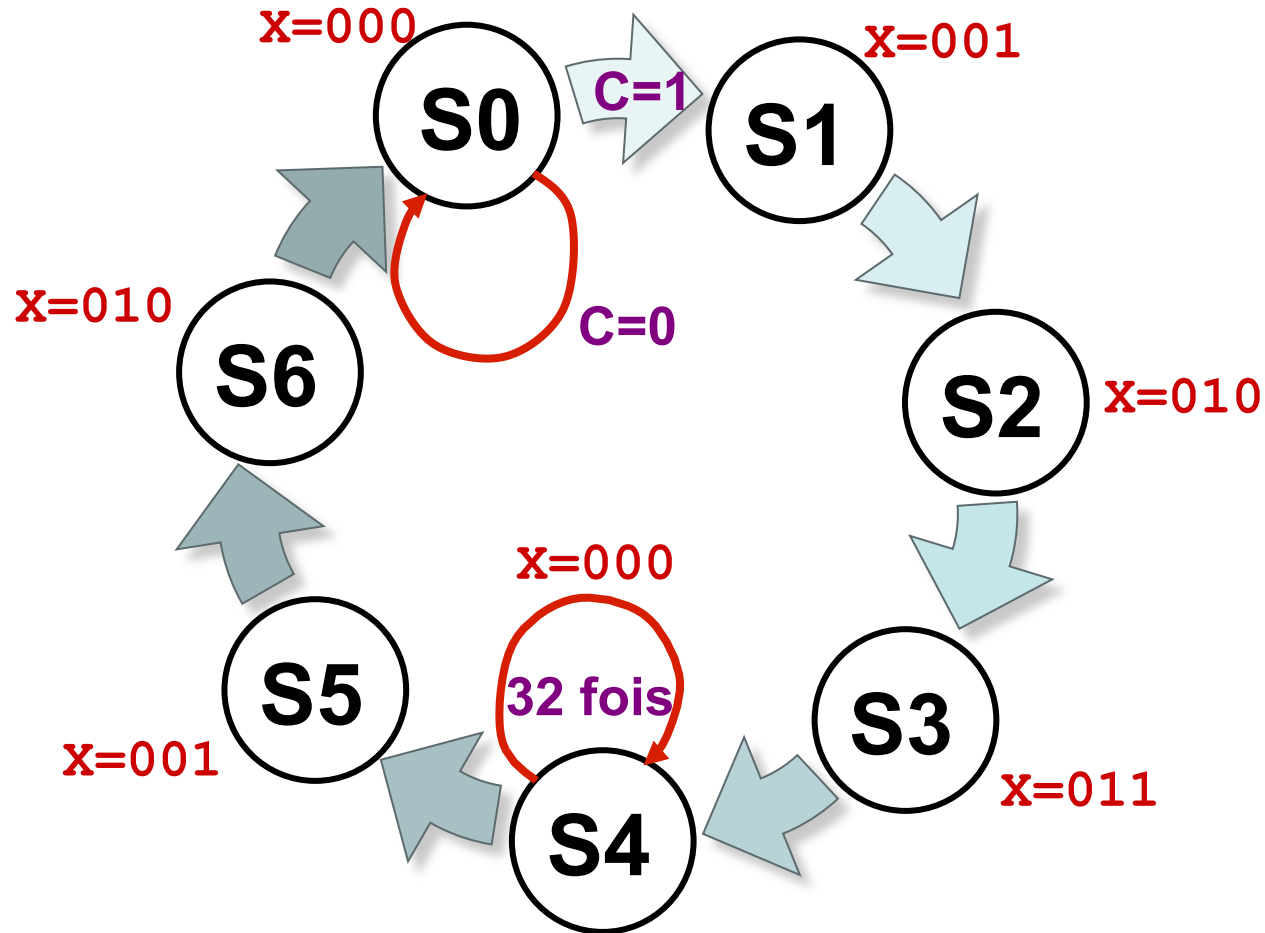

Compteur synchrone
(passage d'un état au suivant sur un front d'horloge)

Partie 4


IMPLÉMENTATION SUR FPGA

Synthèse et Placement/Routage

- ❑ Partie très importante (indispensable)
- ❑ Simulation avec prise en considération des temps de propagation des signaux
- ❑ Génération de la netlist (vhdl, verilog, etc.)
- ❑ Simulation en utilisant la netlist générée (apparition de retards)
- ❑ Résultats différents de la simulation idéale
- ❑ Permet de modifier l'architecture du circuit


Fichier UCF



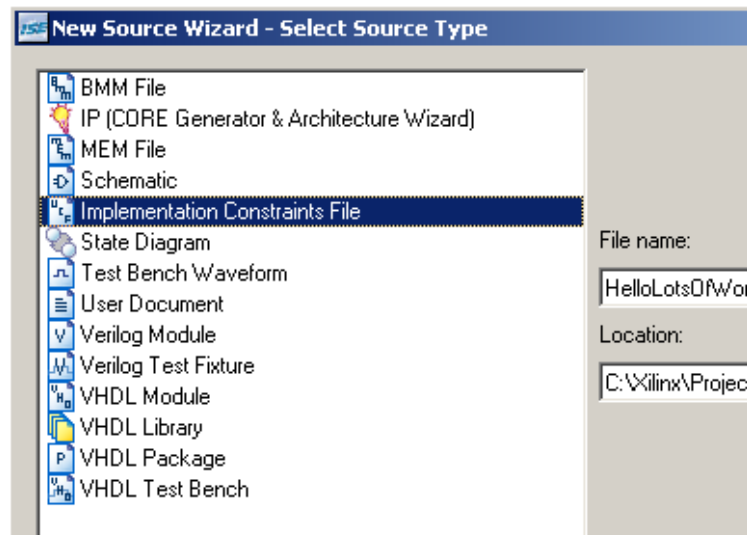
- ❑ UCF : User Constraints File
- ❑ Affecter les entrées sorties d'un module aux pins de l'FPGA
- ❑ Utilisation de la : Data Sheet






```
1 NET "IN<0>" LOC = "P38" ;
2 NET "IN<1>" LOC = "P36" ;
3 NET "IN<2>" LOC = "P29" ;
4 NET "IN<3>" LOC = "P24" ;
5 NET "IN<4>" LOC = "P18" ;
6 NET "IN<5>" LOC = "P12" ;
7 NET "IN<6>" LOC = "P10" ;
8 NET "IN<7>" LOC = "P6" ;
9
10 NET "OUT<0>" LOC = "P15" ;
11 NET "OUT<1>" LOC = "P14" ;
12 NET "OUT<2>" LOC = "P8" ;
13 NET "OUT<3>" LOC = "P7" ;
14 NET "OUT<4>" LOC = "P5" ;
15 NET "OUT<5>" LOC = "P4" ;
16 NET "OUT<6>" LOC = "P3" ;
17 NET "OUT<7>" LOC = "P2" ;
```

Carte Celoxica RC10

 

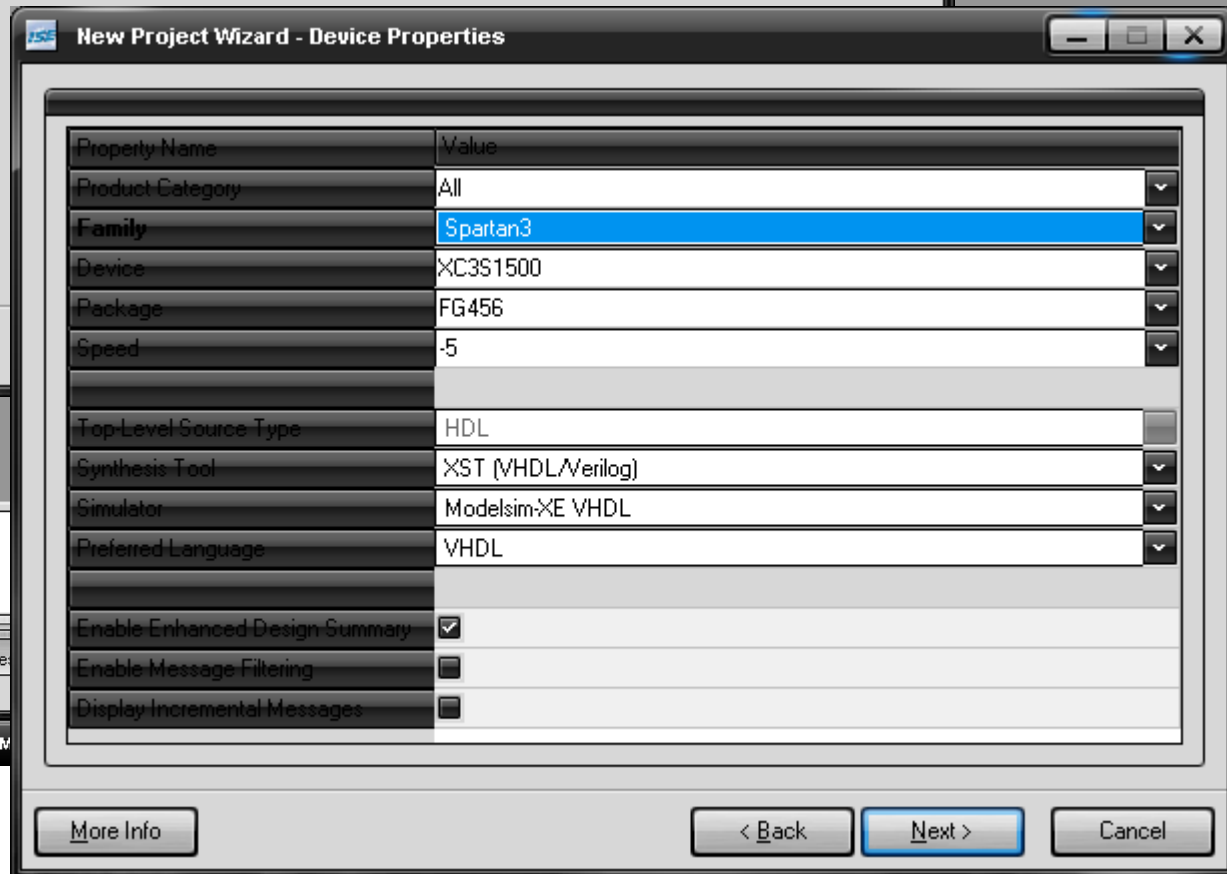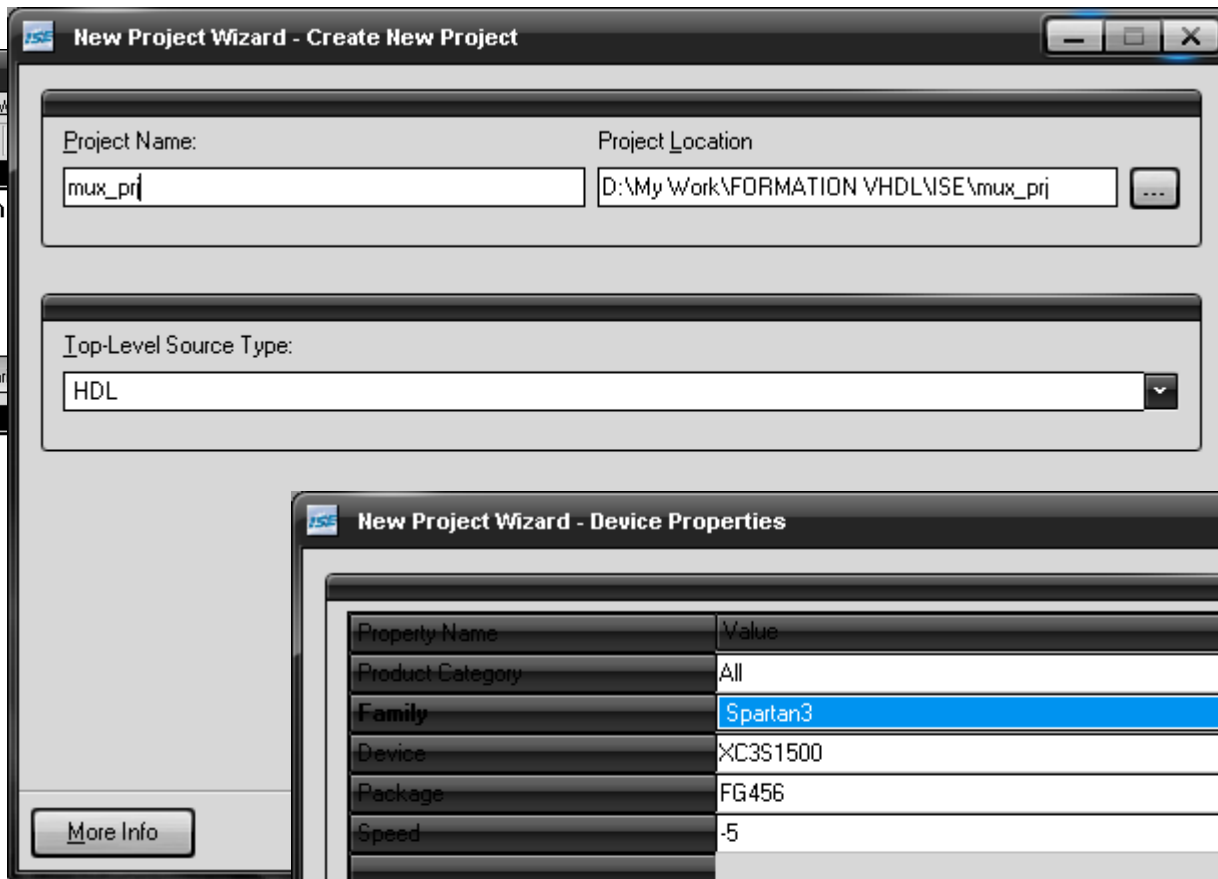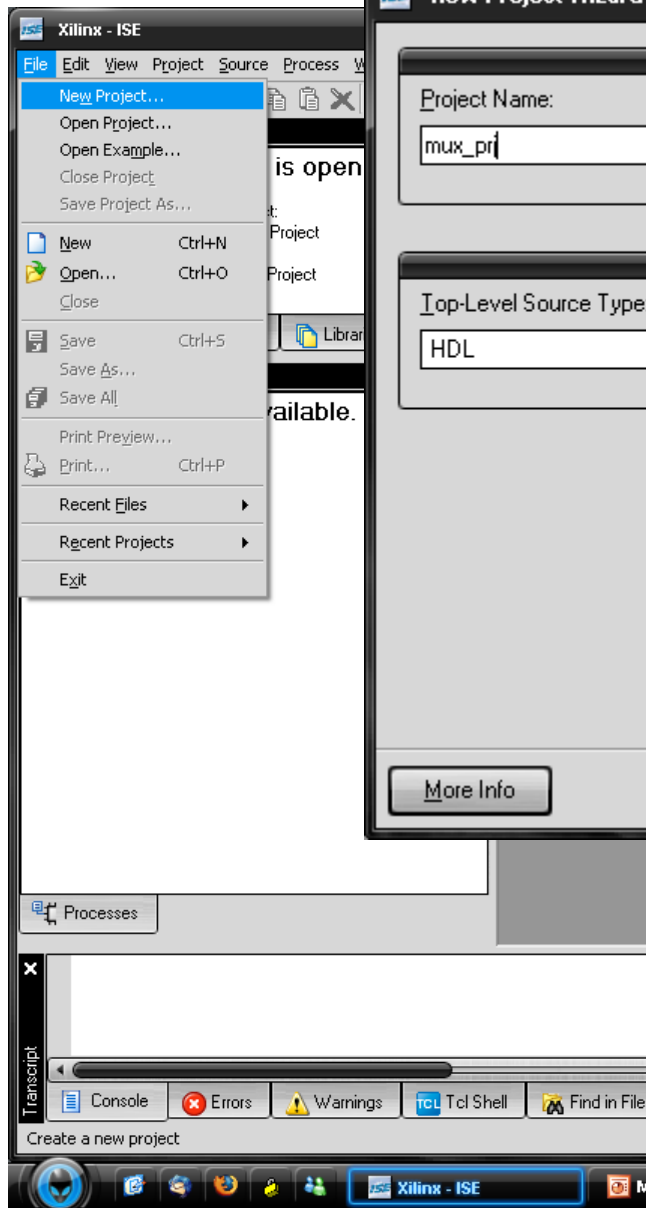

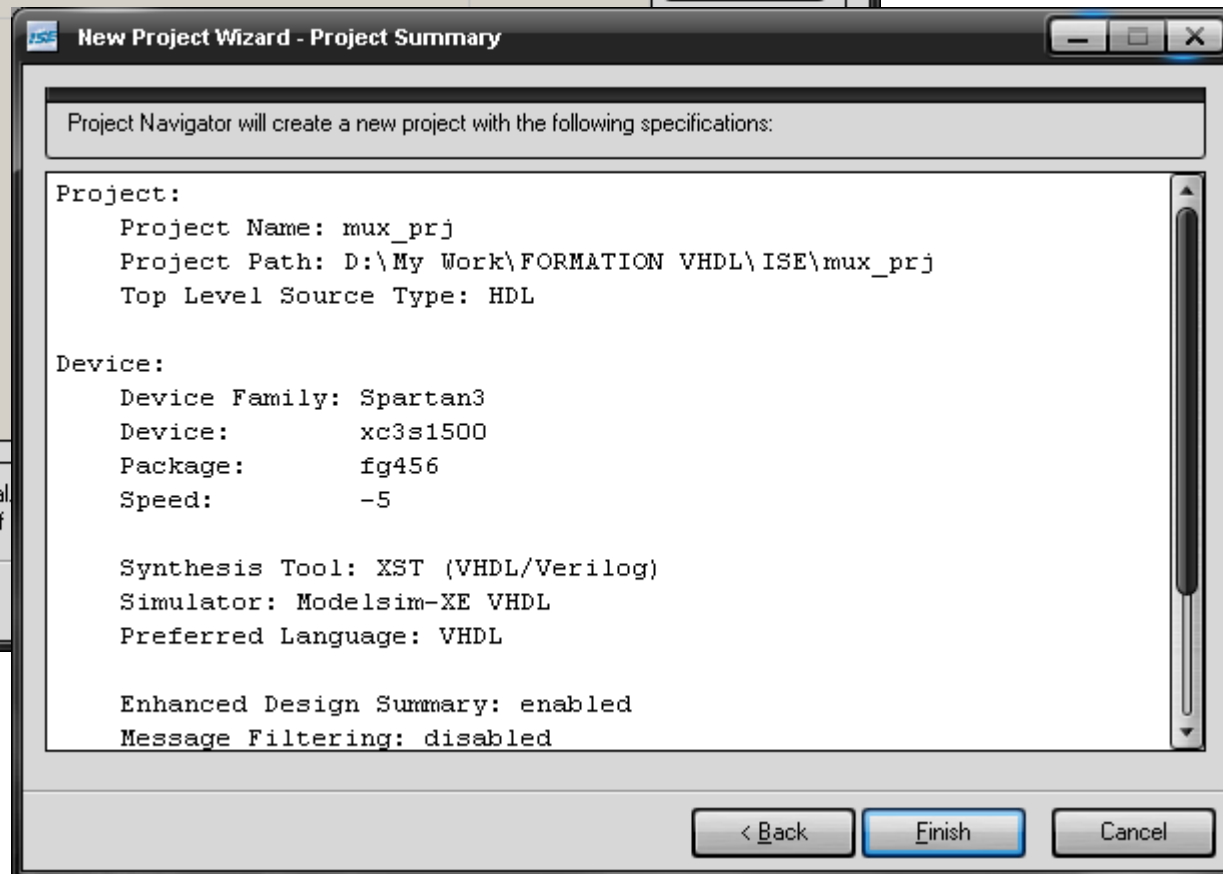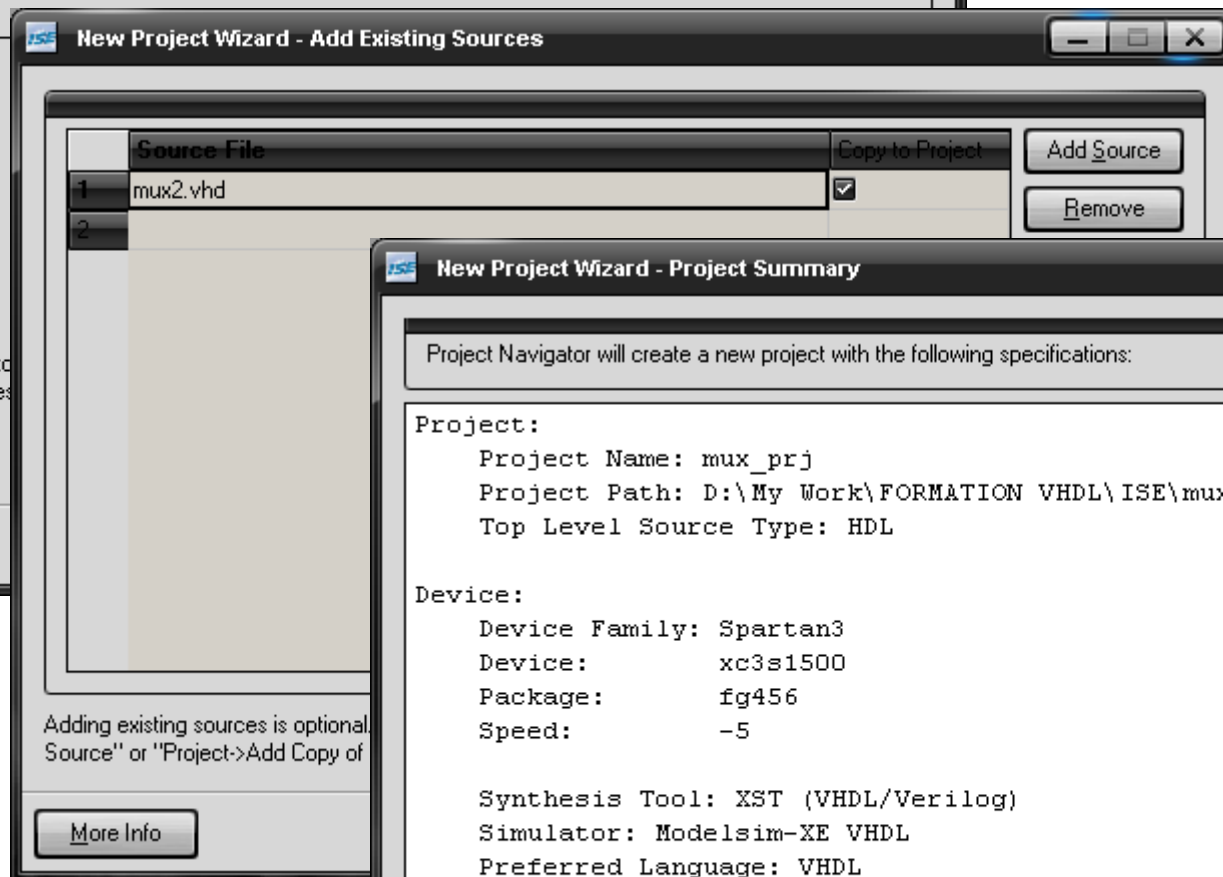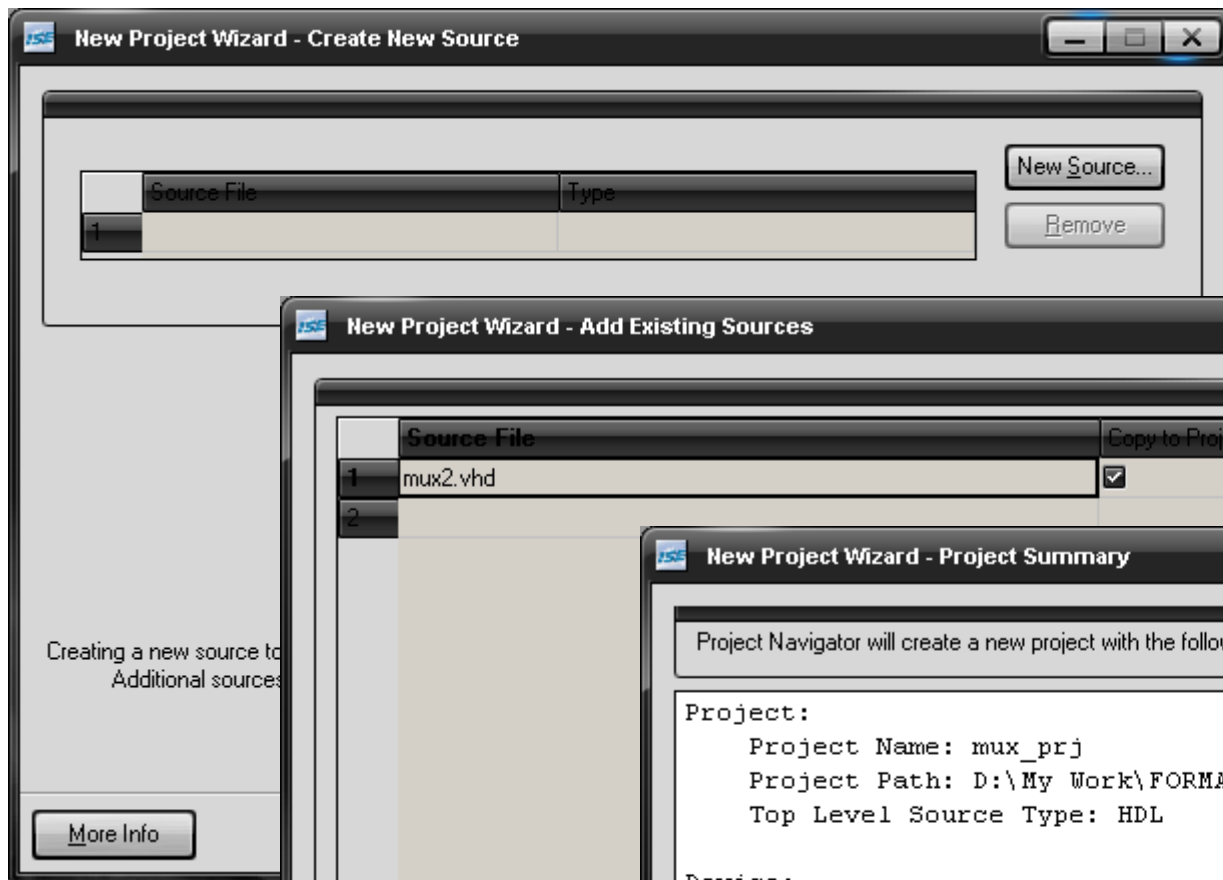

Xilinx - ISE - D:\My Work\FORMATION VHDL\ISE\mu...

File Edit View Project Source Process Window

Sources

Sources for: Synthesis/Implementation

- xc3s1500-5fg456
 - MUX - A (mux2.vhd)

Sources Snapshots Libraries

Processes

Processes for: MUX - A

- Add Existing Source
- Create New Source
- View Design Summary
- Design Utilities
- User Constraints
- Synthesize - XST
- Implement Design
- Generate Programming File

Transcript

Started : "Launching Design Summary"

Console Errors Warnings TCL

Processes

Processes for: MUX - A

- Add Existing Source
- Create New Source
- View Design Summary
- Design Utilities
- User Constraints
- Synthesize - XST
- View Synthesis Report
- View RTL Schematic
- View Technology Schematic
- Check Syntax
- Generate Post-Synthesis Simulation Model
- Implement Design
- Generate Programming File
 - Programming File Generation Report
 - Generate PROM, ACE, or JTAG File
 - Configure Device (IMPACT)

Processes

Processes

Processes for: MUX - A

- Add Existing Source
- Create New Source
- View Design Summary
- Design Utilities
- User Constraints
- Synthesize - XST
 - View Synthesis Report
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simulation Model
- Implement Design
 - Translate
 - Map
 - Place & Route
 - Place & Route Report
 - Clock Region Report
 - Asynchronous Delay Report
 - Pad Report
 - Guide Results Report
 - MPPR Results Utilities
 - Generate Post-Place & Route Static Timing
 - View/Edit Placed Design (Floorplanner)
 - View/Edit Routed Design (FPGA Editor)
 - Analyze Power (XPower)
 - Generate Power Data
 - Generate Post-Place & Route Simulation Model
 - Generate IBIS Model
 - Back-annotate Pin Locations
- Generate Programming File
 - Programming File Generation Report
 - Generate PROM, ACE, or JTAG File
 - Configure Device (IMPACT)

E - D:\My ... synthesis Présentation1.ppt



Xilinx - ISE - D:\My Work\FORMATION VHDL\ISE\mux_prj\mux_prj.ise - [MUX.ngr]

File Edit View Project Source Process Window Help

Sources

- MUX
 - OUTPUT_imp

Processes

No flow available.

Design Summary MUX.ucf Synthesis Report MUX.ngr

Design Objects of Top Level Symbol

Name	Type
MUX	Instance

Properties

No object is selected

Name	Value

Console Errors Warnings Tcl Shell Find in Files View by Category View by Name

Xilinx - ISE - D:\My Work\FORMATION VHDL\ISE\mux_prj\mux_prj.ise - [MUX.ngr] [-12,280]

Xilinx - ISE - D:\My ... Microsoft PowerP... mux_prj 22:19

Xilinx - ISE - D:\My Work\FORMATION VHDL\ISE\mux_prj\mux_prj.ise - [MUX.ngr]

File Edit View Project Source Process Window Help

Sources

- MUX
 - OUTPUT_imp

Processes

No flow available.

Design Summary | MUX.ucf | Synthesis Report | MUX.ngr

Design Objects of MUX

Name	Type
SEL	Net
SEL	Pin

Properties

No object is selected

Console | Errors | Warnings | Tcl Shell | Find in Files | View by Category | View by Name

[488,-56]



Xilinx - ISE - D:\My Work\FORMATION VHDL\ISE\mux_prj\mux_prj.ise - [MUX.ngr]

File Edit View Project Source Process Window Help

Sources

- MUX
 - OUTPUT_imp

Processes

No flow available.

LUT Dialog

LUT3
INIT = E4

Schematic TruthTable Karnaugh Map


OK Help

AppletViewer : Source.class

Applet

Applet démarré.

Cas de monocircuit

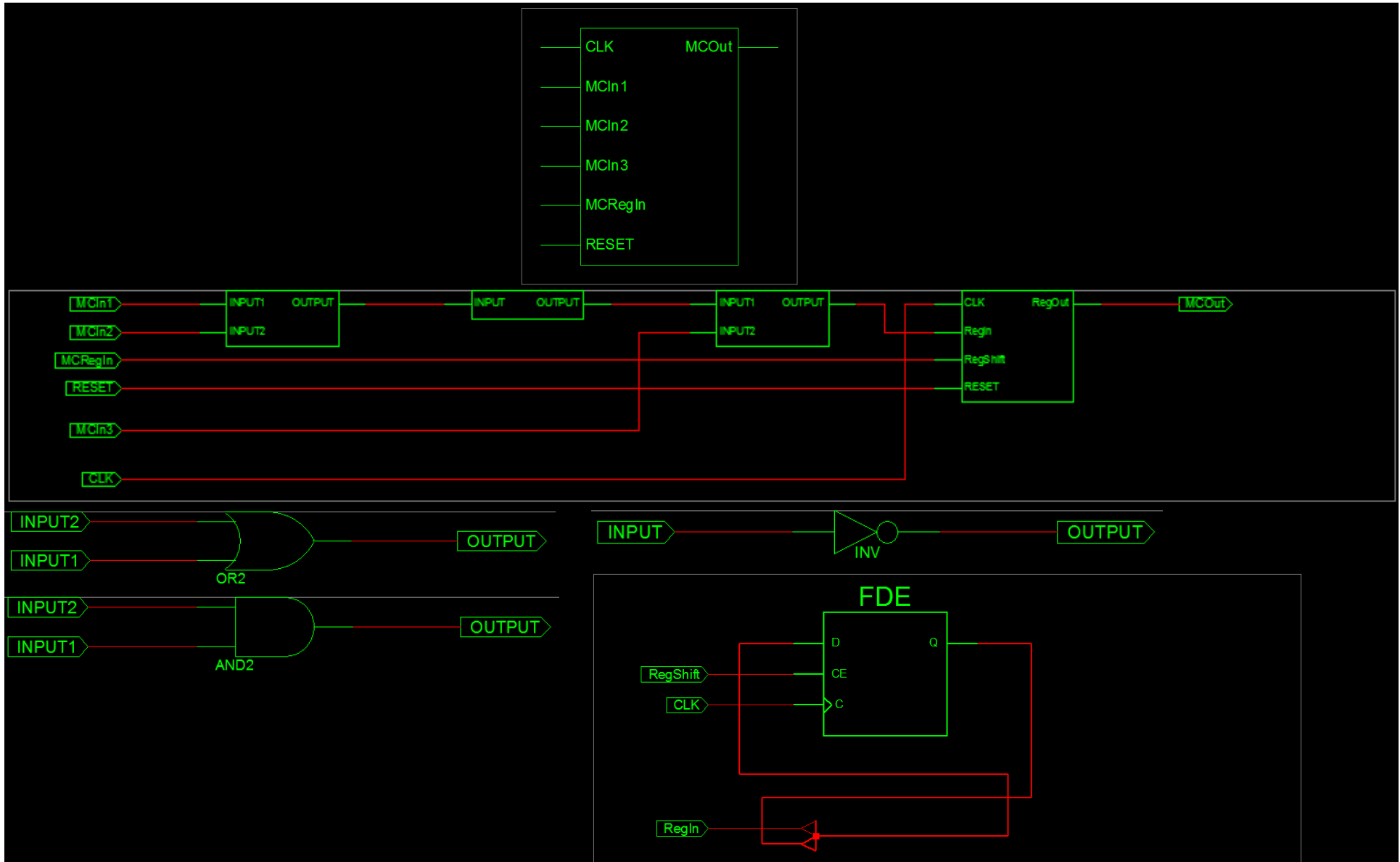



iIMPACT Programmation du FPGA

Release V...
Application...
Registrati...
Copyright...
All rights re...

The screenshot displays the iIMPACT software interface. The main window has a menu bar with File, Edit, View, Operations, Output, Window, and Help. The File menu is open, showing options like New (Ctrl+N), Open Project... (Ctrl+O), Open Configuration Archive... (Ctrl+H), Initialize Chain (Ctrl+I), Save Project (Ctrl+S), Save Project As... (Ctrl+J), Save Configuration Archive..., Export Project To CDF, Recent Files, New Log File..., and Exit. Below the menu is a Modes section and an iIMPACT Processes section. The Transcript window at the bottom shows the following text:


```
// *** BATCH CMD : setMode -acecf  
// *** BATCH CMD : setMode -acempm  
// *** BATCH CMD : setMode -pff
```

An iIMPACT Project dialog box is overlaid on the main window. It contains the text "I want to" and two radio button options:

- load most recent project [text field] [Browse...]
- create a new project (.ipf) [text field: default.ipf] [Browse...]

There is also a checkbox labeled "Load most recent project file when iIMPACT starts". At the bottom of the dialog are OK and Cancel buttons. The Windows taskbar at the bottom shows several open applications, including FORMATION VHDL, Microsoft Power..., ModelSim SE PLU..., and iIMPACT.

Programmation du FPGA

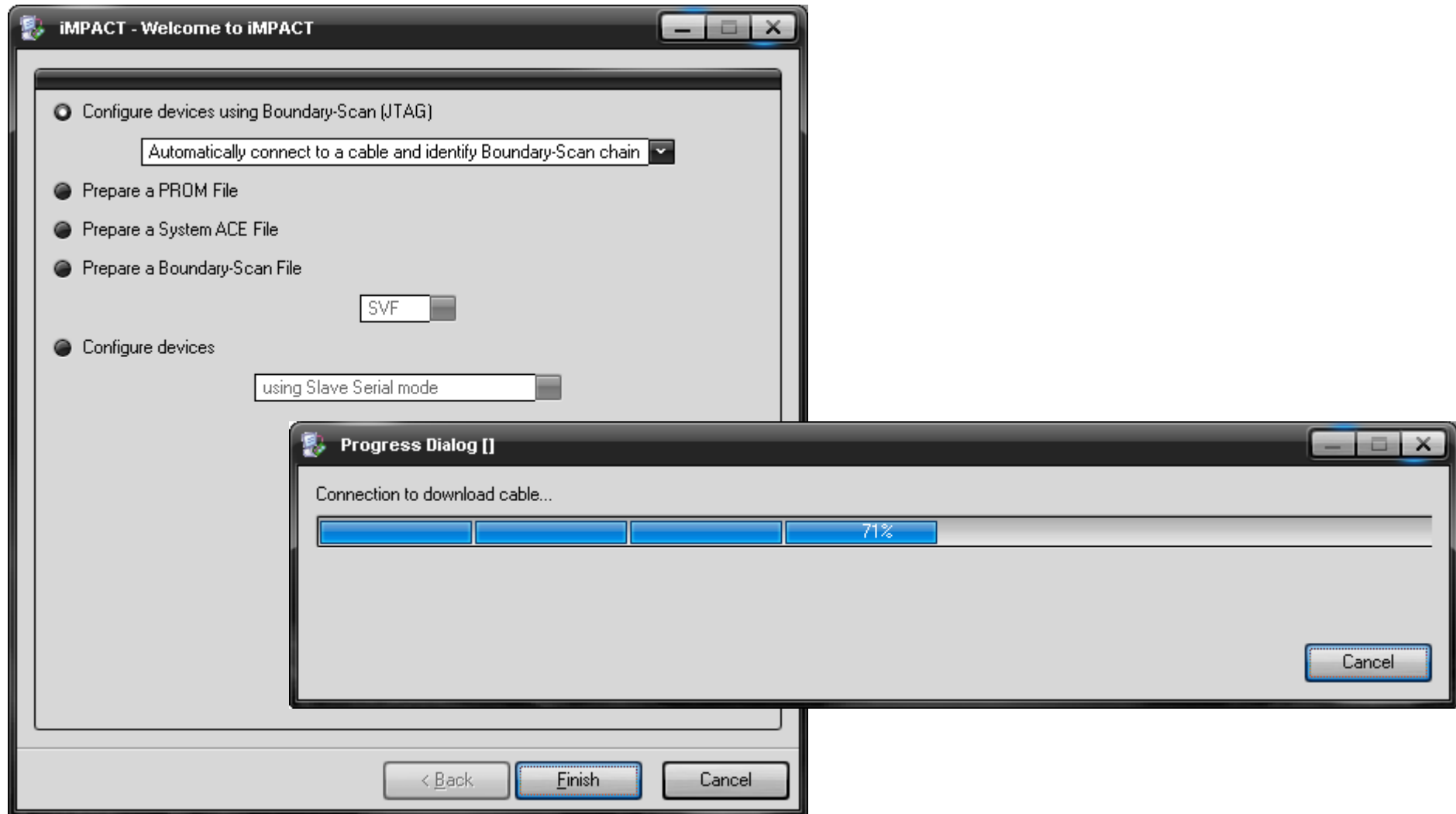

Merci